

Cowtown ARC  
'Buildathon' 2023


Project #3:

## QRP – ATU

HF 10w Antenna Tuning Unit



Richard W5ARH / VK2ARH  
vk2arh@att.net

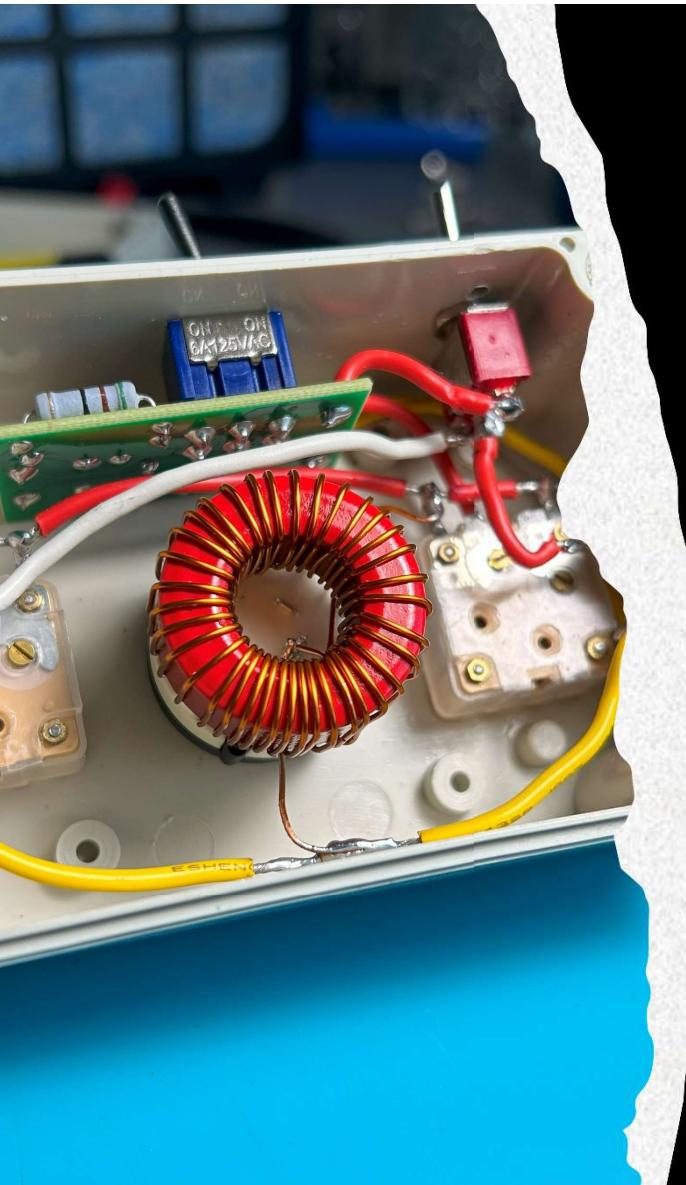

# Presentation - Thursday October 19<sup>th</sup> 7:00pm

## Buildathon 2023 Project #3

# Agenda

- ATU's
    - What is it ?
    - **Basic** Theory of Operation
    - Practical Use
    - Automatic or Manual
  - Buildathon Refresh
  - Project #3 – QRP ATU
    - Kit Introduction
    - Construction Process Outline
  - Questions
  - Kit Collection

## **Supported Build Program – Saturday 21<sup>st</sup> October 9:00am**

**Breakfast Day Break Café 8:00am for those interested**



## ATU – What is it ?

An **antenna tuner** is an electronic device inserted into the feedline between a **radio** and its antenna.

Its purpose is to optimize power transfer by matching the impedance of the radio to the signal impedance at the end of the feedline connecting the antenna to the transmitter. Wikipedia

An antenna tuner or antenna tuning unit is a network of variable inductors and capacitors that can be altered to counterbalance the effects of the inductive and capacitive elements of the antenna with the aim of making the antenna appear as a resistive load of  $50\Omega$ .

<https://www.electronics-notes.com/articles/antennas-propagation/antenna-tuning-tuner-unit/what-is-an-atu-basics.php>

Their basic purpose is to ensure that the antenna system impedance matches that of the transceiver to ensure maximum transfer of power between the radio and the antenna.

**The ATU does not change the radiation efficiency of the antenna, just enables more power to be transferred to it, without damaging the radio**





# Basic Theory of Operation

An antenna tuner or antenna tuning unit is **a network of variable inductors and capacitors** that can be **altered to counterbalance the effects of the inductive and capacitive elements of the antenna** with the aim of making the antenna appear as a resistive **load of  $50\Omega$** .

<https://www.electronics-notes.com/articles/antennas-propagation/antenna-tuning-tuner-unit/what-is-an-atu-basics.php>

The theory is complex and ‘not for the feint hearted’ ... BUT  
We can simplify the concept

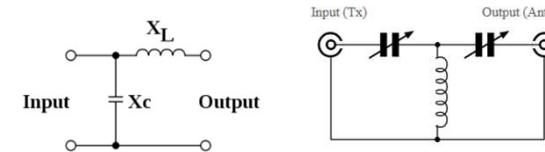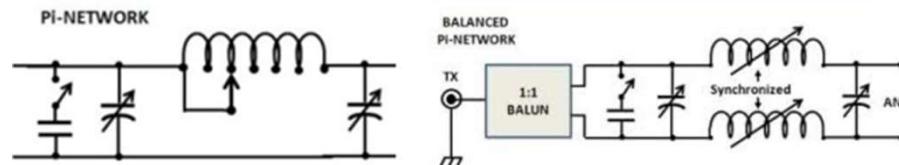A component will exhibit a complex impedance when there is a phase shift between the voltage across it and the current through it. A resistor has no phase shift between the current and voltage across it.



Reflection and Transmission Coefficients  
for an Ideal Transformer

$$\begin{aligned}
 & \text{Transmission Line 1 (Ininitely long)} \quad \text{Z}_0 = Z_a \\
 & \text{Transformer (Lumped-Element)} \quad 1:N \quad V \text{ ratio} \\
 & \quad \quad \quad 1:N^2 \quad Z \text{ ratio} \\
 & \text{Transmission Line 2 (Ininitely long)} \quad \text{Z}_0 = Z_b \\
 \\
 & j\Gamma_2 = ((Z_b(N^2)) - Z_a) / ((Z_b(N^2)) + Z_a) \rightarrow \Gamma_2 = (Z_a(N^2) - Z_b) / (Z_a(N^2) + Z_b) \\
 \\
 & T_F = N^2(Z_b(N^2)) / ((Z_b(N^2)) + Z_a) \rightarrow T_F = (2^2 Z_a(N^2)) / (Z_b + (Z_a(N^2)) / N) \\
 \\
 & T_R = (2^2 Z_a(N^2)) / (Z_b + (Z_a(N^2)) / N)
 \end{aligned}$$

$$\begin{aligned}
 & \text{Transmission Line 1 (Ininitely long)} \quad \text{Z}_0 = 50 \\
 & \text{Transformer} \quad 1:2 \quad V \\
 & \quad \quad \quad 1:4 \quad Z \\
 & \text{Transmission Line 2 (Ininitely long)} \quad \text{Z}_0 = 50 \\
 \\
 & \Gamma_2 = -0.6 \rightarrow \Gamma_2 = 0.6 \\
 \\
 & T_F = 0.8 \rightarrow T_R = 0.8
 \end{aligned}$$



<https://www.blueridgeamateurradio.com/antenna-tuner-science/how-antenna-tuners-work>

[Antenna tuner - Wikipedia](#)

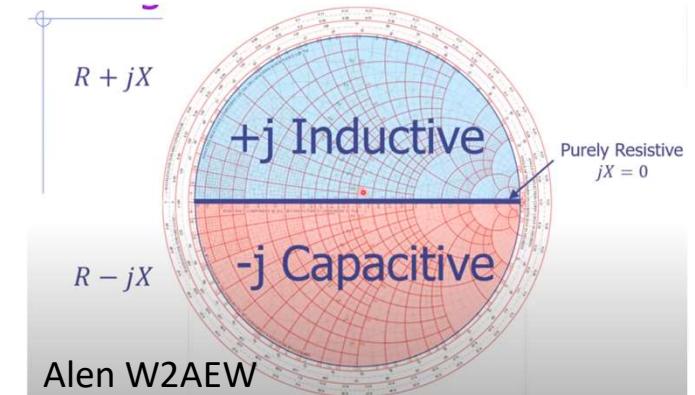
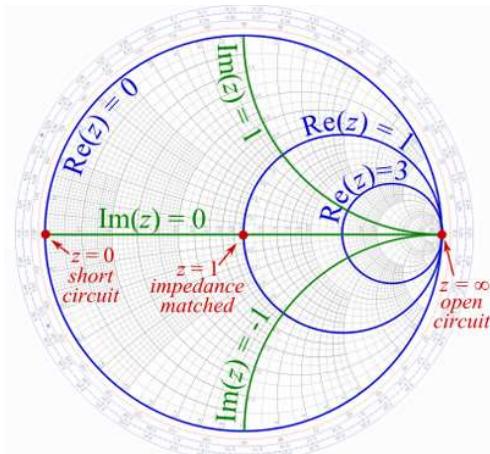
# Visualizing the Impact on a Smith Chart



- The Smith chart is used to display the resistive and reactive portions of a **component's complex impedance** ( $z = \infty R + jX$ ) versus frequency
- Complex impedance changes with frequency ... a point on the chart plots a single frequency – a line plots a 'sweep'
- The **aim is to adjust the inductive and capacitive impedance of the antenna system so that we get a purely resistive  $50\Omega$  match.**


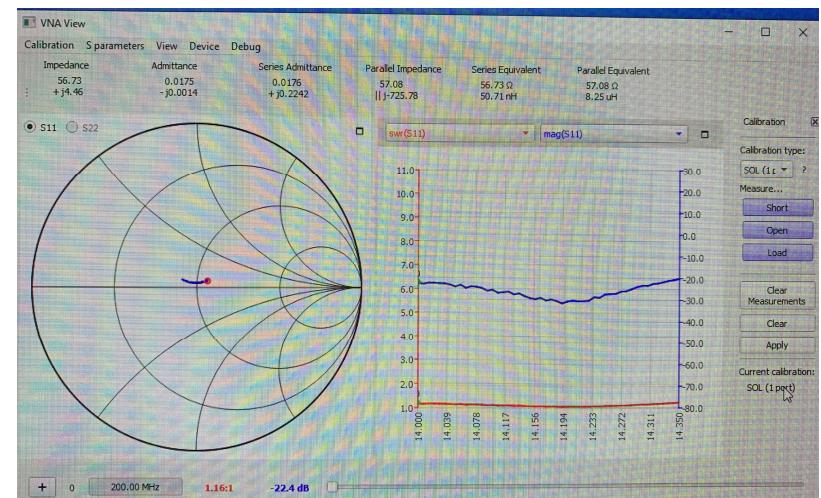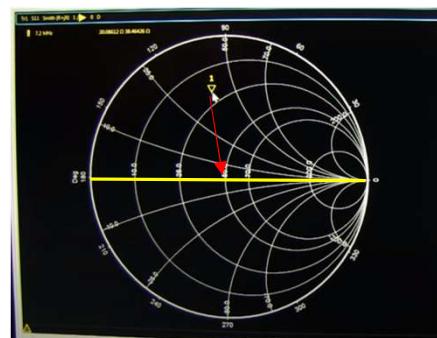
<https://www.youtube.com/watch?v=f8wJ0io95RE>



# Visualizing the Impact on a Smith Chart




Great results can be achieved with the humble Nano VNA see Alen W2AEW's video



[https://www.youtube.com/watch?v=xa6dqx9udcg&list=PL4ZSD4omd\\_AzQ7T0Dt4zTBW8sHLQHjqMQ](https://www.youtube.com/watch?v=xa6dqx9udcg&list=PL4ZSD4omd_AzQ7T0Dt4zTBW8sHLQHjqMQ)



# Tuner Types

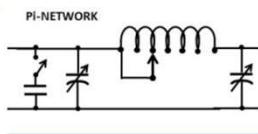

## Tuner types

There are 4 classic antenna tuner types that are still used in all of today's modern antenna tuners. The following sections describe the pluses and minuses of each type and provides proof of efficiency for each.

A tremendous amount of additional information can be found on this very comprehensive Wikipedia page: [https://en.wikipedia.org/wiki/Antenna\\_tuner](https://en.wikipedia.org/wiki/Antenna_tuner)

### The PI Network

The PI Network circuit, as depicted above, is found in both antenna tuners and as tank circuits in older tube style transmitters and linear amplifiers. The PI network is considered to be a low-pass filter and normally contains 3 tunable components. Generally the design calls for fairly large variable capacitor values and as such can be expensive to build. A concern for the Amateur Radio Operator is that the PI network, just like the T network, can produce resonance at more than one set of component values. The difference between the settings results in higher or lower efficiency and thus power lost to heating.

Component values generally range from 10-500 pF for the variable caps and 2-20uH for the roller inductor or tapped coil.


The circuit depicted above is unbalanced in that the "hot" side is treated differently than the "shield" side of the tuner. Basically it's not symmetrical and thus better suited for coax to coax antenna tuners.

#### Pros:

- Broad banded, able to match a wide range of impedances
- Can be modified to allow for the selection of lower value variable components by adding additional fixed components to the input side of the network
- Simple to implement
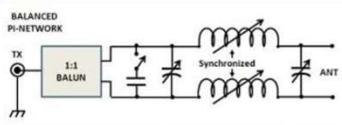
#### Cons:

- More knobs means more time required to find a good match
- More than one resonance point can be found using different component values
- If tuned to an incorrect resonance point, power loss due to heating of the roller inductor will result
- Power loss due to heating in this network is higher than that of the L network and significantly more than that of the symmetric PI network
- 500 pF capacitors can be large and expensive



## The Symmetric PI Network

Definitely the most complicated tuner in terms of the number of components and their relationship to one another. The Symmetric PI network implementations are rare in the tuner world.

The symmetric PI-Network is definitely the most complicated design, although the fully switchable L network can be just as difficult to implement. This network topology is rare in the Amateur Radio world, due to the cost of assembling one of these units. Four separate components are required, including 2 large roller inductors and 2 variable capacitors. Additionally, this is a fully balanced network, meaning that the components are mirrored from side to side. Due to symmetric construction of this network, the entire matching section must be floated above ground (disconnected from the case) and because of this stray capacitance can play a factor in tuner performance.

Note that in this and other symmetric designs, a current balun (1:1) is required to achieve equal currents on both sides of the network and must be installed BEFORE the tuner instead of AFTER the tuner. Because the balun is installed before the tuner, the number of toroids required to provide the correct amount of common mode current impedance protection is reduced as the toroid is not subject to the wild voltages that may be encountered on the feed line side of the network.

Component values for the capacitors range from 10-300pF and the roller inductors have a value of 2-20uH. The roller inductors in this network must be linked together through a belt system, which further complicates the implementation of the device and adds to the additional expense of the unit.

Additional capacity may be required on the output side when attempting to create a match on 160 with an antenna that is "short" for that band - i.e., less than 1/2 wavelength long. This is usually accomplished by adding switched capacitance in shunt to the output.

Symmetric PI network tuners can be a bit difficult to tune, but the resonant match will generally be very good. The most important fact about the symmetric tuner is that it is incredibly efficient. Where other tuners may lose up to 10% of input power due to heating, the symmetric tuner loses a fraction of that with no heating problems.


**Pros:**

- Provides a very good match on all frequencies where a "long" antenna is utilized - i.e., 1/2 wavelength or better
- Extremely efficient (See the section below for proof)
- Provides excellent common mode current stopping power when used in the configuration illustrated above
- Specifically designed for balanced antenna systems

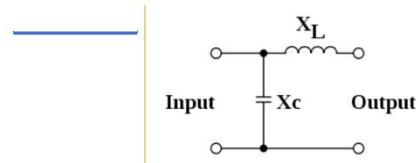**Cons:**

- Difficult to implement
- Requires more components and thus is more expensive
- Specifically designed for balanced antenna systems
- Improper construction can lead to stray capacitance issues


<https://www.blueridgeamateurradio.com/antenna-tuner-science/different-types-of-tuners>



## L-Network

L network tuners are very popular and can be found in all production tuners. The PI network tuner described above is really just 2 L network tuners connected back to front. The L network tuner is found in all electronic designs and is used, obviously, to convert either a low impedance to a high impedance or a high impedance into a low impedance.

## TenTec 238 - 2Kw

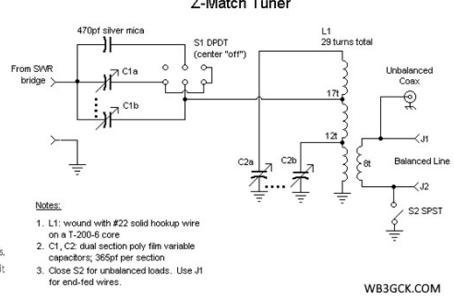

# Z Match – Popular QRP ATU




## Advantages

- Matches balanced loads without the use of lossy baluns.
- Being a parallel resonant circuit, the Z-match can provide some band-pass filtering for your receiver and harmonic attenuation for your transmitter.
- A well-designed Z-match tuner has a high Q and is more efficient (less lossy) than other types of tuners.
- The fixed inductor simplifies construction (no taps or rollers needed).
- Using a toroid inductor and some small poly-film variable capacitors, the Z-match can be built into a very compact package. Appeals to QRPs.
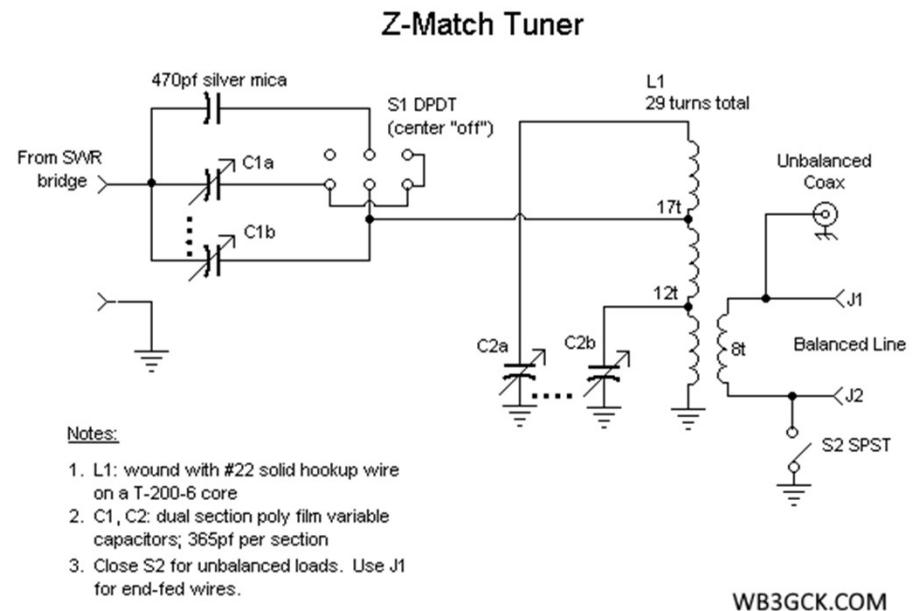
## Disadvantages:

- Tuning is usually very narrow and can be a bit touchy
- The range of impedances that can be matched is not as great as in other designs, such as the "T" configuration.




WB3GCK.COM
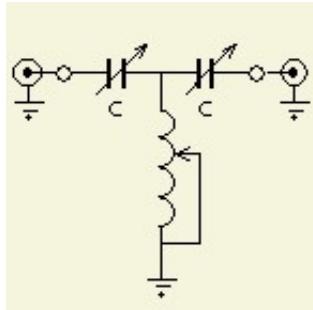
# The Cowtown ATU uses the T Network




The T network configuration is found in the vast majority of commercial antenna tuners.

- It provides **good matching capabilities across a wide range of frequencies** and can be configured with either a tunable inductance (roller inductor) or a fixed switchable inductance (tapped coil).
- T network is really just 2 L networks fixed back to back with a common inductor.
- This design allows for easier matching of the **50Ω load on the input side as well as wide range matching on the load side**.
- The network illustrated above is unbalanced and works well in a coax to coax implementation.



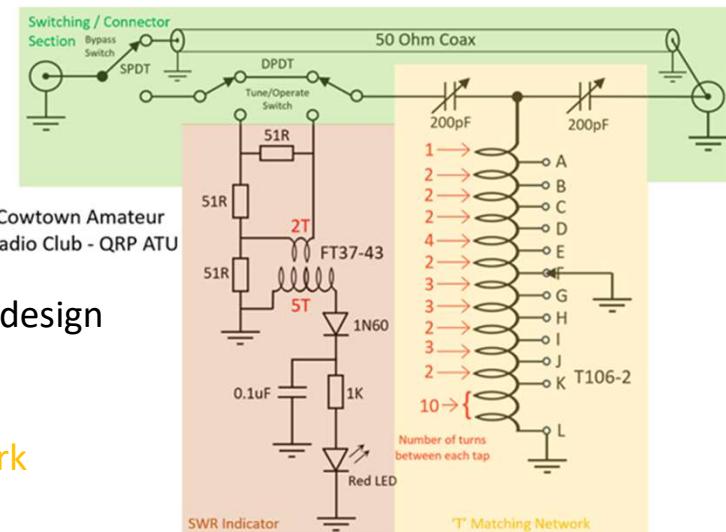- 3 Components to the design
- **Switches**
  - **SWR Indicator**
  - **T Matching Network**




# Lets Take a Closer Look at the ATU Circuit



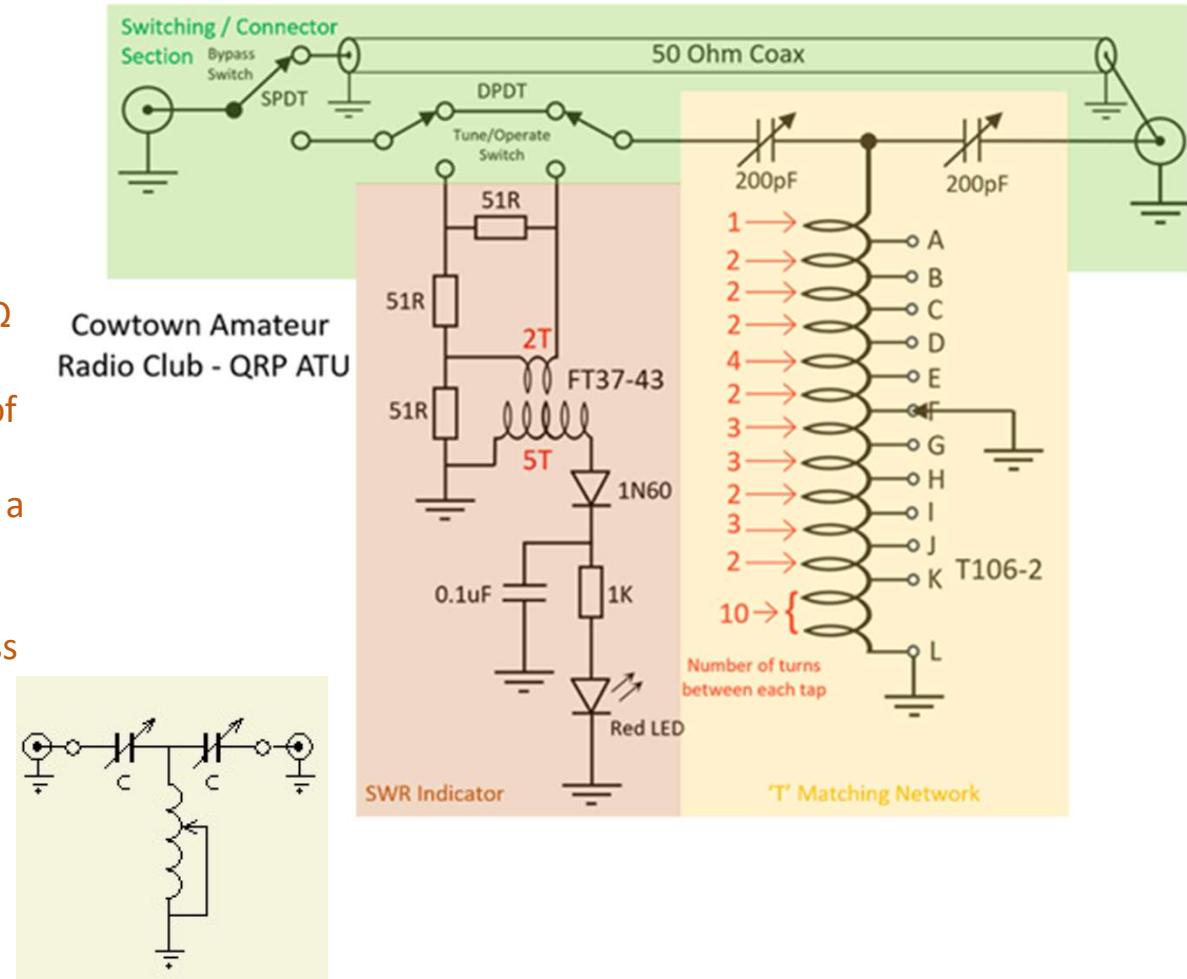
## 3 Sections to the design

- Switches
  - Bypass
  - Tune / Operate
- SWR Indicator
  - Resistive Wheatstone Bridge SWR Sensor
    - When the antenna impedance is  $50\Omega$  the bridge is in balance and no voltage appears across the primary of the toroid.
    - As the impedance departs from  $50\Omega$  a proportional voltage appears across the transformer and lights the LED.
    - The SWR Bridge introduces a 6dB loss when in use, so is switched out for operation.
- T Matching Network
  - Utilizes two  $200\text{pF}$  Polyvaricon capacitors
  - 12 Tap (variable in steps) inductor


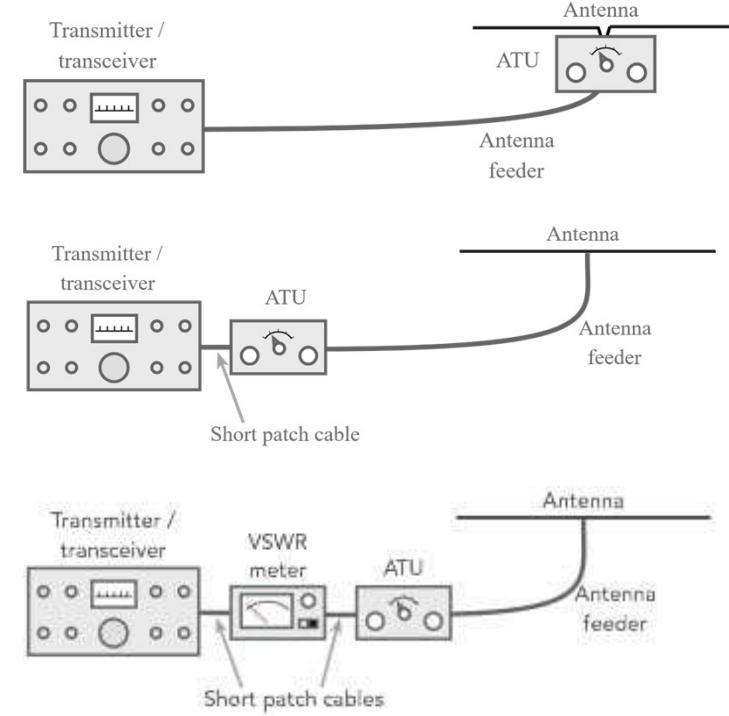
## Where to Locate the ATU

- The ideal position for the location of the antenna tuner is at the point where the antenna is fed by the feeder. In this way, the antenna can be matched to the feedline and all the way through the system there are good matches, and low SWR levels.
- BUT .... Not very practical – so more practical to locate next to the radio.
  - It is a common misconception that a high standing wave ratio itself causes loss. This is not true... When a high standing wave ratio exists, this results from power being reflected back along the feeder as a result of a mismatch. When it enters the antenna tuner, it is reflected back along the feeder to the antenna where a proportion is radiated and some reflected back along the feeder again.
  - With an SWR of 2:1, 11% of power is reflected and 89% is radiated. **If you can transfer more power to the antenna, you get 89% of the extra power radiated.**
- It is worth placing a VSWR meter in the line to monitor the actual level of standing waves seen by the transmitter. Note: a separate meter may not be required if one is incorporated into the transmitter or the ATU, unless it is more convenient to monitor the level separately.



<https://www.electronics-notes.com/articles/antennas-propagation/antenna-tuning-tuner-unit/what-is-an-atu-basics.php>



## Types of ATU – Automatic / Manual




~ \$215



~ \$285



~ \$310

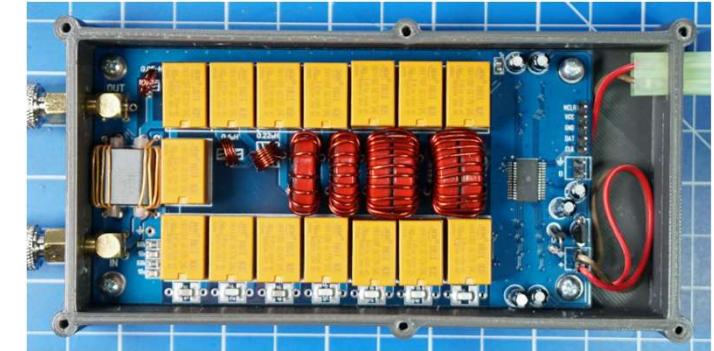

~ \$120



QRP – 10w

~ \$30



QRP – 5W

~ \$60



100W



# 'Buildathon' 2023

The Buildathon set out to provide three practical kits this year:

- Project #1:  
EFWH Antenna



- Project #2:  
QRP Digital Mode HF Transceiver (ADX)




- Project #3:  
QRP Manual ATU



The ATU project complements the previous 2 projects and provides a working QRP capability for shack and field operations

The project introduces the following Elements:

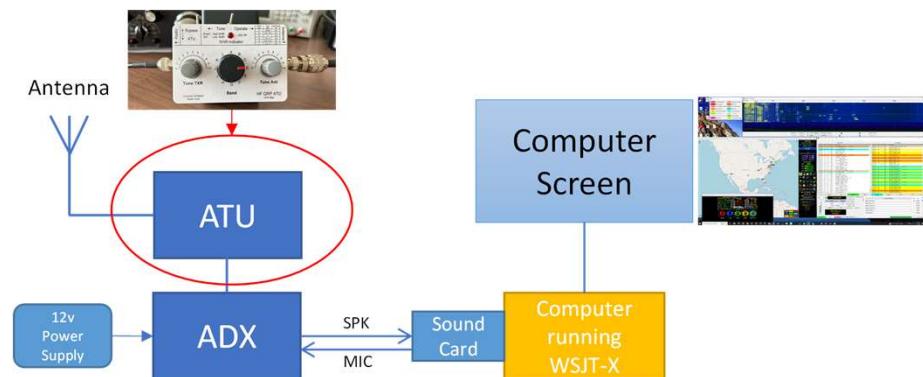
- Hardware Mounting and Integration
- Tapped Inductors
- Emphasis on mechanical as well as electrical construction
- New theory and operating concepts


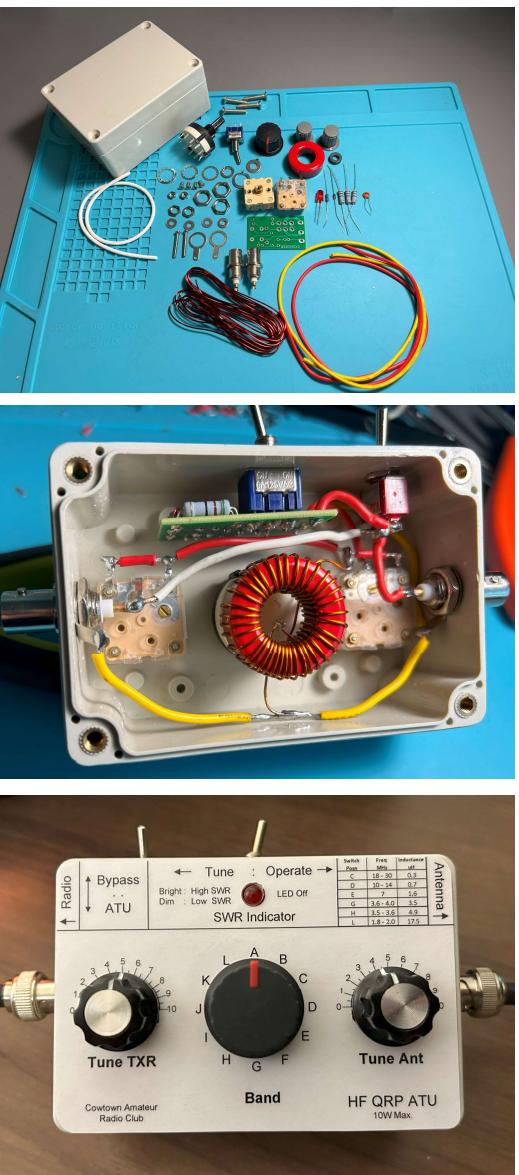
# 'Buildathon' 2023

- Project #3: HF QRP Antenna Tuning Unit – Lets take a closer look at the build process







## Buildathon Project #3 - QRP ATU



- Provides a HF Antenna Tuning Unit (ATU) capable of supporting QRP radio's
  - up to 10w<sup>max (SSB)</sup>, and is a great little pocket sized and 'fit for purpose' ATU
  - It works well
- Is utilizes a 'T' matching network consisting or a switched inductance and two variable capacitor – matches across a wide range of frequencies
- Has built in SWR indicator which can be used when tuning the antenna with the ATU
- Cowtown Kit incorporates:
  - ATU bypass switch
  - Templates to facilitate the correct drilling and placement of components, and a high-quality panel overlay
  - Detailed construction manual (similar in detail to the Cowtown ADX manual) see: <https://github.com/VK2ARH/Cowtown-ADX-Project>
  - Corrected all the errors with the original 'Chinese kit'
    - Identified by Carol KP4MD in her excellent video on the topic → <https://youtu.be/JceLhTV28oI?si=10w3uxhJedoQut1m>

# Schematic Diagram

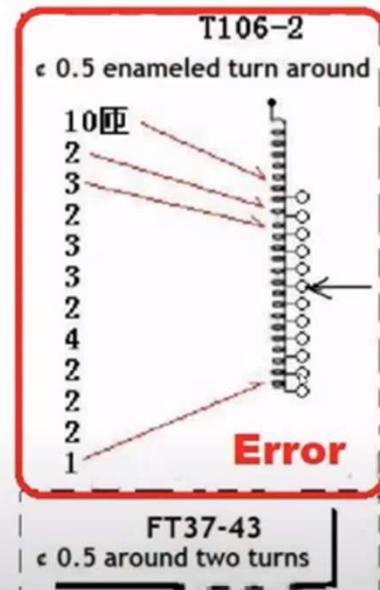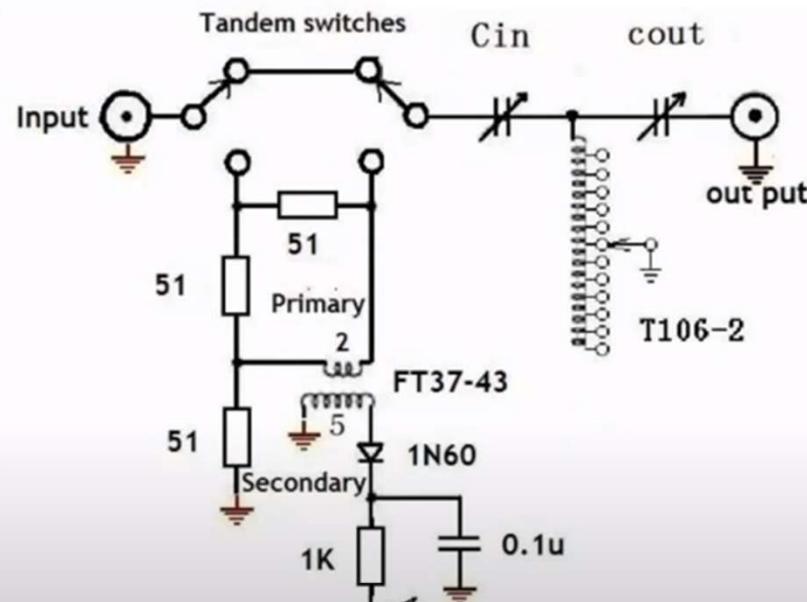

The error with that is that you need to fine tune the inductor at minimum inductance. So this was inverted.

Chinese QRP Antenna Tuning Unit



9:26 / 22:11 • The Circuit Description >



Fixing a Chinese "QRP Manual Days" Antenna Tuner Kit



KP4MD  
984 subscribers

Subscribe

171



Share





Download

Clip

Save


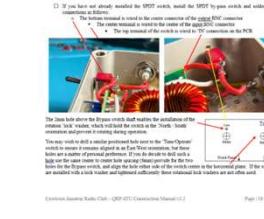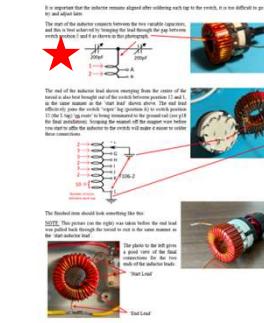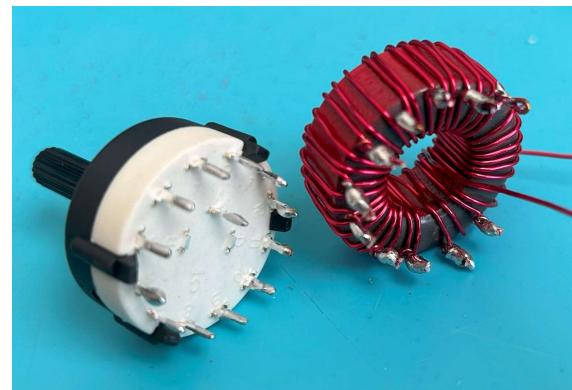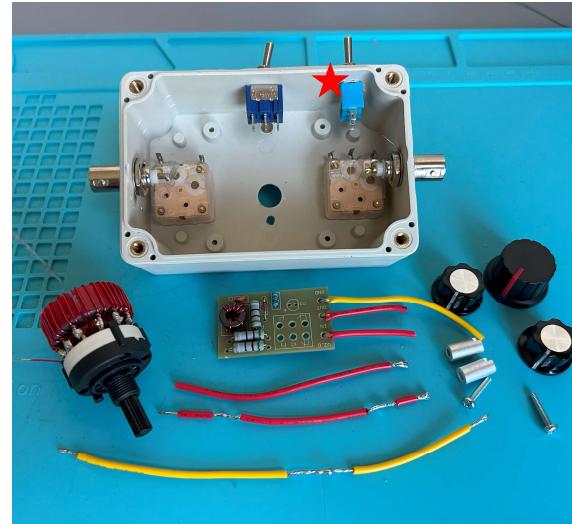
# The Cowtown Kit – Differences from the Original Chinese ‘Manual Day’ Kit



Cowtown Amateur Radio Club - QRP ATU Construction Manual v1.2

Page 14 / 21



Cowtown Amateur Radio Club - QRP ATU Construction Manual v1.2

Page 15 / 21



Cowtown Amateur Radio Club - QRP ATU Construction Manual v1.2




Page 16 / 21

**23 Page Construction Manual**  
Corrected all the errors with the original kit

<https://github.com/VK2ARH/Cowtown-ATU-Project>
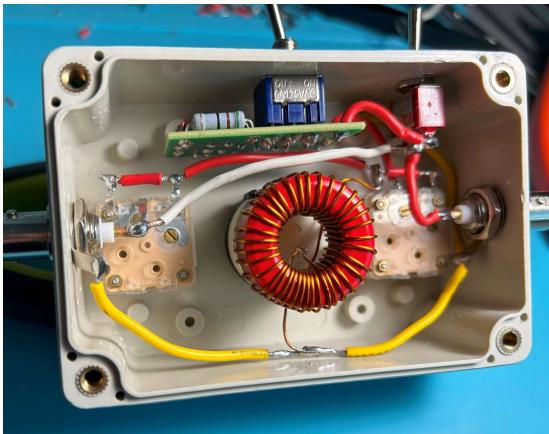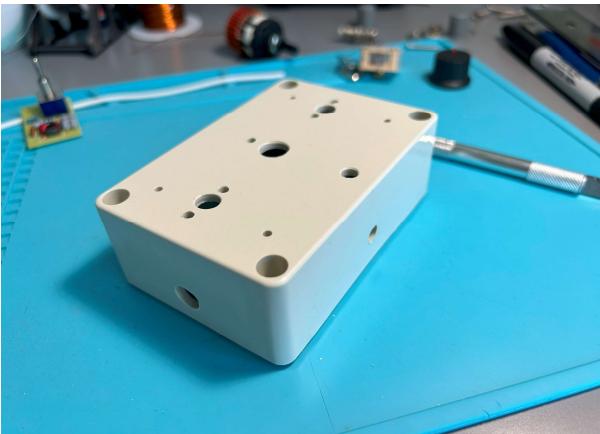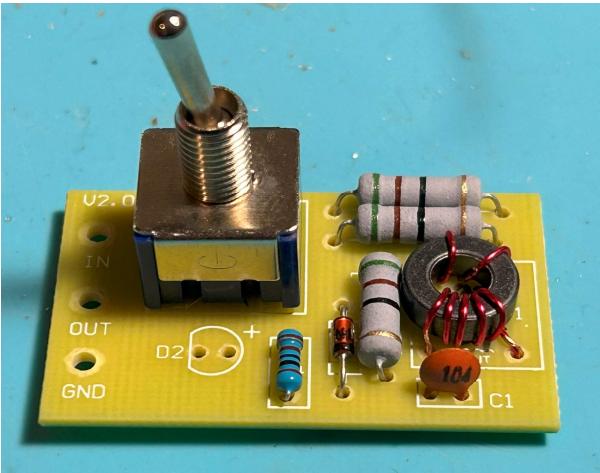
# 'Buildathon' 2023

- Project #3: HF QRP Antenna Tuning Unit – Stages of the Build




# Drilling Template and Panel Overlay



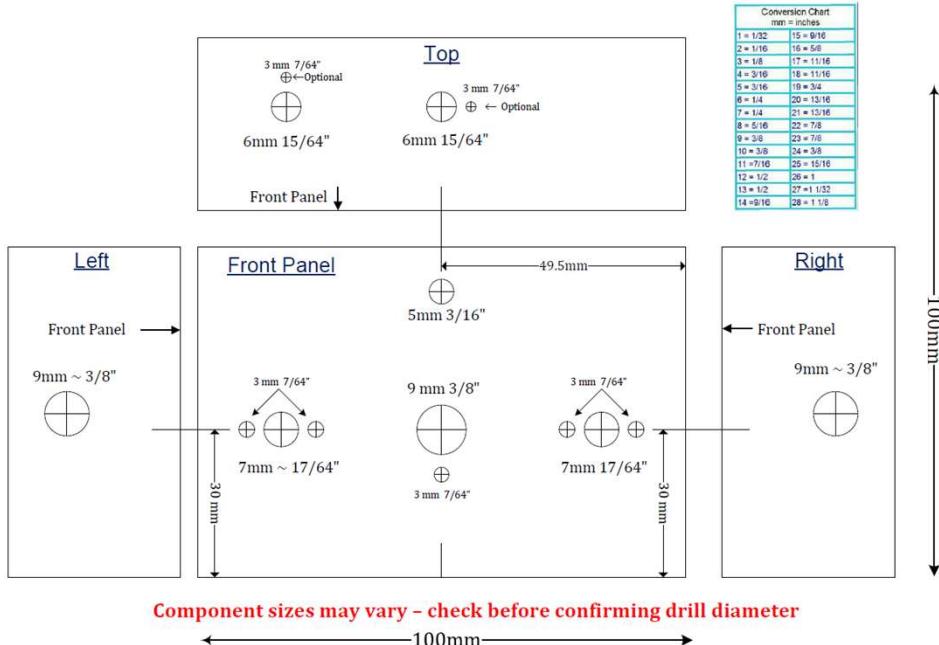
## Cowtown Amateur Radio Club QRP ATU Drilling Template


When Printing ensure that the 100mm Lines are scaled to exactly 100mm



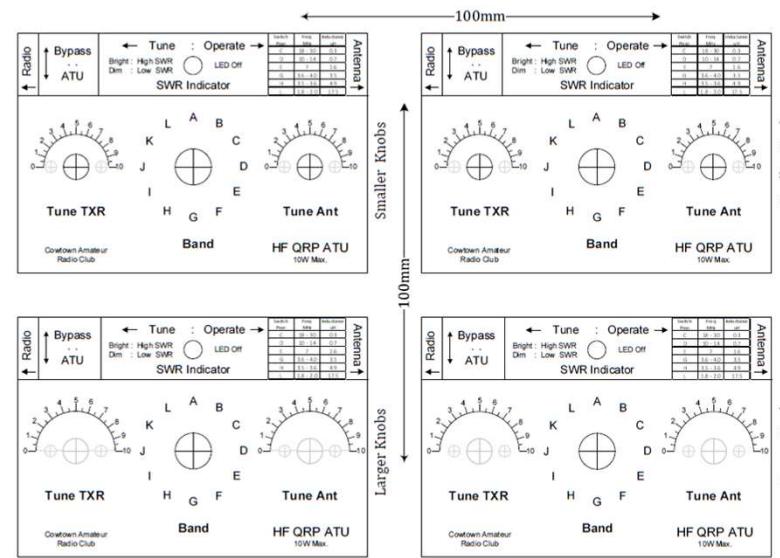When Printing ensure that the 100mm Lines are scaled to exactly 100mm




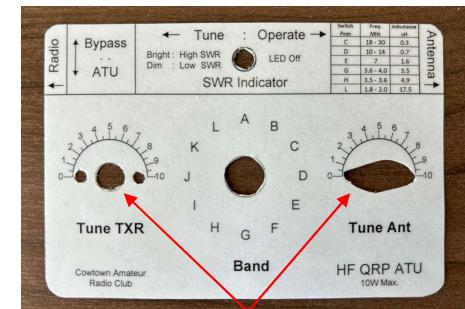
Two Sizes of Scale provides for different sized tuning knobs




Tuning Knobs cover the holes so either option OK

Cut out and laminate - then stick to front panel with double sided tape after carefully removing holes with a sharp modeling knife


# Preparing the Enclosure

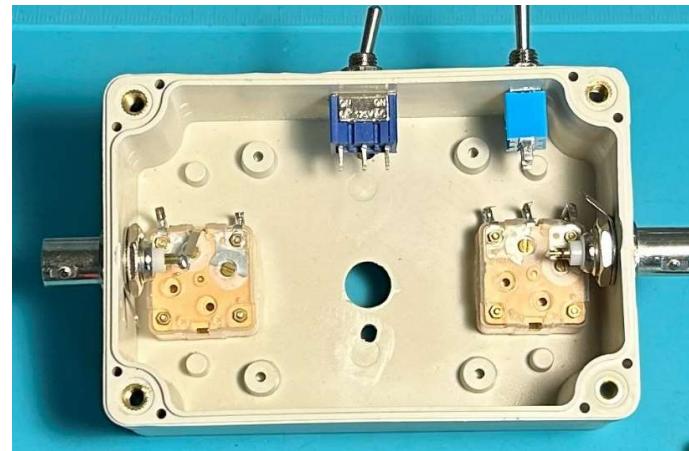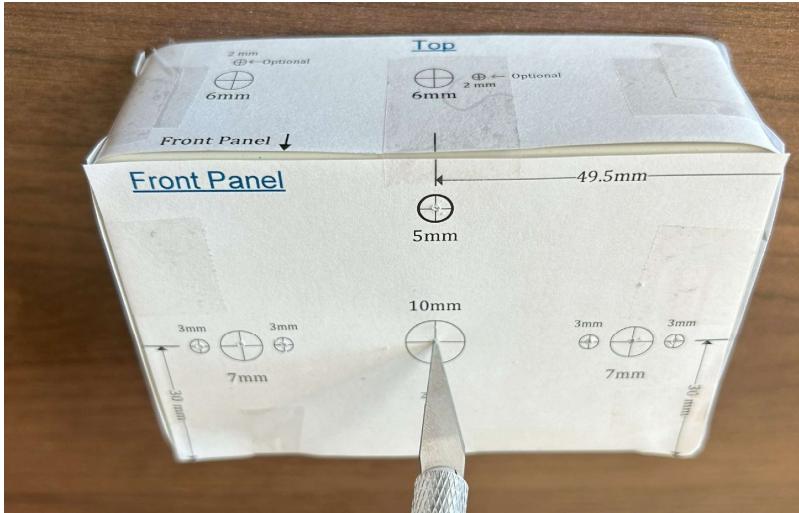


# Building the Tapped Inductor

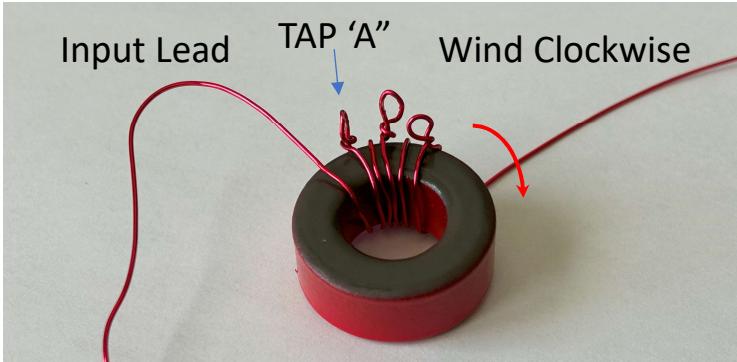

## Starting the Wind

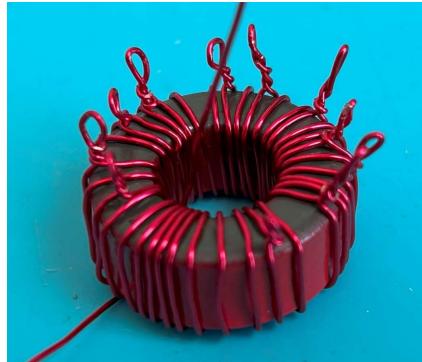

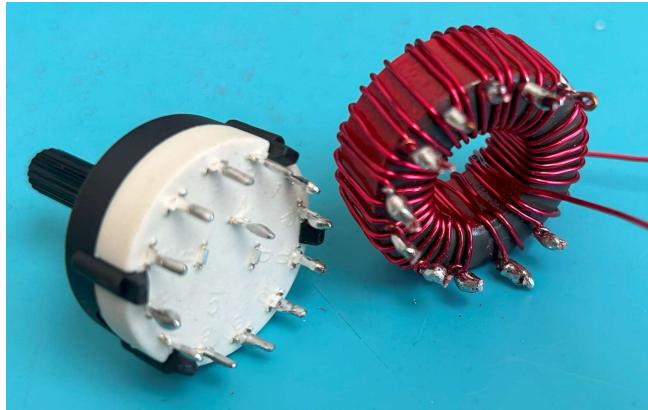The finished Inductor  
Keep it tight – twisting the taps helps



Scrape and ‘Tin’ the Taps and the switch lugs



Spread the Taps to Align with the lugs  
on the switch and progressively solder  
to the switch

### Winding the Main Inductor

Winding the main 36 turn, 12 tap inductor and then soldering it to the 12-position switch is probably the most demanding element of the ATU build, it's a little tedious but not complicated. Anyone who has successfully wound a toroid for the LPF's as part of the ADX project or an EFWH Antenna [User](#), has the capability of winding this inductor. It just requires a little time and care.

There are a couple of techniques to consider for winding the inductor. The first

If you are in your chosen method, start at 17 turns after the 'H' tap and 15 turns before it. You will require approximately 1 1/2" (37mm) of wire, so you would need to fold the wire back over itself to make a loop. Then, starting at the 'H' tap, make a 'U' turn to the left at the 'H' tap and the longer wire of one direction starting with the fold as the tap at position 'H' and then work in reverse at 37 turns G making a 'U' turn to the right at the 'G' tap and the longer wire of one direction starting in the same direction and then using the shorter section of wire taps downward through positions J, I, K and add the required number of turns and taps downward as you go.

carefully winding the inductor and inserting the taps as I went. I also made sure that the names of the turns you have completed on the diagram are correct so that you can follow along.

Start by inserting the end through the center of the twisted fold, then make sure back to form a loop (this becomes tap A) which you then twist and then continue to wind twice through the toroid and form another loop which will become tap B. Continue this process until you reach the number of turns required and then mark in red on the diagram above until you have completed all 12 turns. The finished inductor will look something like this:

**NOTE:**

- the position of the tap is on the outer edge of the toroid.
  - Twisting the tap also pulls any loose winding tighter.
  - Make ever effort to pull the wire tight against the toroid when winding to make a more tightly wound inductor.
  - Ensure the wire is not crossed at any stage.
  - Spread the taps evenly around the toroid to ensure that they align with the bags on the 12.5Ω resistors.
  - Leave a short length of wire on the first and last turn to enable connection to the rest of the ATU in the hexagon.

We are aiming to end up with an inductor switch that looks something like this, so keep this in mind when winding the inductor and mounting the inductor on the switch in the next step:



#### Mounting the Inductor on the 12 Position Switch

The next task is to mount the tapped inductor onto the 12-position rotary switch. Start by tinning each tap to enable easy soldering to the lugs on the 12-position switch. There are two techniques you can choose here:

- The first is to unwind each leg by hand, strip off the enamel, then re-wrap it again and lay the tape. The problem with this method is that it is very time consuming and difficult to wrap the ends of the turns from the outer legs inwards. Another problem is that the tap is fiddly when winding the inductors, each of your taps are likely to be different lengths... will complicate aligning and soldering the leads to the switch legs which will mean continuity through the entire inductor.
  - The second (shown in the photo) is to cut each leg to the required length and then wrap and clamp off the ends. Then you can strip the tape off the top of each leg a little and then wrap the ends of the turns around the top of the legs. This way the ends of the turns are all at the same height. The downside is that the leads will be completely sand away and a length of soft copper tape on this can easily be bent around the legs.

This second technique using the Dremel to sand the enamel away from the tap will still leave enamel in the twist crevasses and although the inductor wire that is exposed will be tinned, you are likely to end up with insulated gaps between other


**NOTE:** When tinning the inductor pins, the wire of the inductor is a good conductor so draw heat away from the solder end of the tap in some instances – HOWEVER this is overcome when you solder the tap to the tinned switch lug in the next step – so don't panic if you find breaks in the inductor continuity when testing the continuity through your inductor taps after tinning.

**NOTE:** When tinning the insulation strip, use **WAVE** or **SHIELDED** to prevent heat away from the metal joint, so ensure you have a suitably rated soldering iron that can deliver the required heat to achieve a good 'tin'.


The 12-position rotary switch can easily be damaged if you apply too much heat to the 'position lugs' on the switch



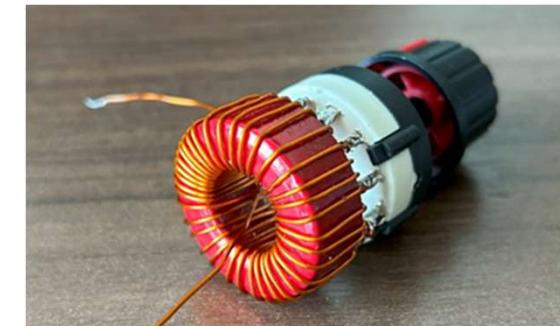the manual  
/ mark off the turns  
as you go.



# Final Assembly

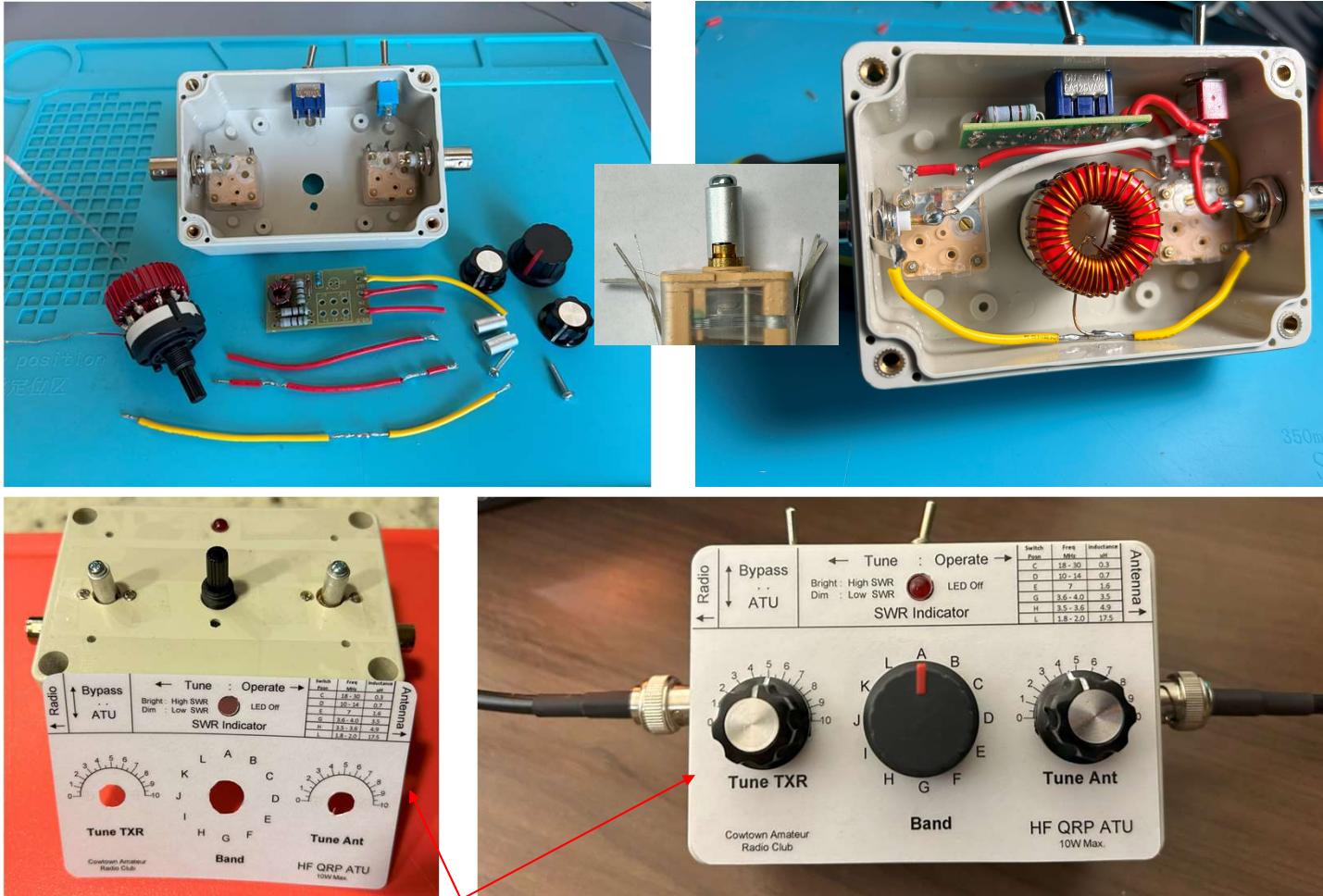

- This is a mechanically challenging project
- You'll learn a lot if you haven't done this sort of project before
- Take your time
- Build in stages
- Check your work at each stage
- It's not a race
- Take pride in your work
- Enjoy the results

# The ATU Project

## 'Buildathon' Event #3




### Logistics and Details:

- Cost of the kits is \$15** - now available for collection
- 20 Kits were reserved – additional Chinese kits can be sourced from Amazon, but these kits don't have the Cowtown Extra's.
- I have a small number of extra tuning capacitor 'knobs and shafts' if anyone needs them. \$3 per set of 2. I also have spare panel overlays and drilling templates

An Amazon product listing for a "1-30 MHZ Manual Antenna Tuner kit for HAM Radio QRP DIY Kit". The listing shows a photograph of the kit components, including a blue printed circuit board, various capacitors, resistors, and a small motor. The price is \$15.81, marked down from \$19.81. It includes a 30-day return policy and Prime Two-Day delivery. The item is listed by "Zerone Store" with 64 ratings and 5 answered questions. The product description includes details about the antenna tuner's performance, such as a tuning range of 30-300 Ohms and its use for QRP communication.

- All documentation can be downloaded and printed from:
  - <https://github.com/VK2ARH/Cowtown-ATU-Project>
  - Club Groups.io site – Buildathon Project Files

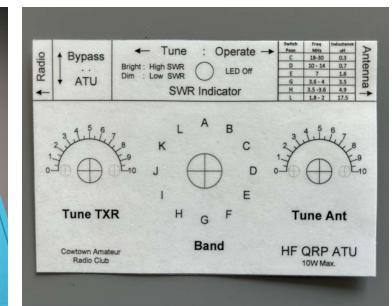**Supported build session on Saturday October 21<sup>st</sup> commencing with breakfast next door to the club at 8.00am**



# QRP – ATU Manual Antenna Tuning Unit

Documentation from the Cowtown Amateur Radio Club (Fort Worth, Tx)  
ATU Project and can be found here:

<https://github.com/VK2ARH/Cowtown-ATU-Project>

Contacts for the Cowtown Amateur Radio Club:

[info.cowtownarc@gmail.com](mailto:info.cowtownarc@gmail.com)

<https://www.cowtownarc.org/home>

